

E3-277 Introduction to Integrated Circuit Design

Lab Assignment 3

Submitted

by

Group No 19

Dhruv Patel-27096

Priyanshu-26201

Nimer Qadir-27224



under the guidance of

PROF.GAURAB BANERJEE

**DEPARTMENT OF ELECTRICAL COMMUNICATION
ENGINEERING**

INDIAN INSTITUTE OF SCIENCE

BENGALURU - 560012

Contents

Contents	i
List of Figures	iii
0.1 Two-Stage Op-amp	1
0.2 DC Testbench results	5
0.3 AC Testbench results	8
0.4 Transient Testbench analysis	9
0.5 Include the individual responses in the report to the following:	11
0.5.1 Dhruv Patel	14
0.5.2 Priyanshu	21
0.5.3 Nimer Qadir	24

List of Figures

1	A basic two-stage operational amplifier.	1
2	Two-stage Opamp	4
3	DC operating points	4
4	Opamp with $V_{in} = V_{cm}$	5
5	Opamp with $V_{in} = V_{id}$	5
6	CMR Curve	6
7	VTC Curve with derivative	7
8	AC Response for uncompensated opamp	8
9	AC response of compensated opamp	8
10	Positive step response of compensated opamp	10
11	Negative step response of compensated opamp	10
12	Step response of uncompensated opamp	11

0.1 Two-Stage Op-amp

In this homework, you are to design a basic two-stage CMOS operational amplifier (op-amp), as shown in Fig.1, for the specifications given in Table 1. The op-amp consists of a differential input stage (M_3 and M_4) driving a current mirror load (M_1 and M_2) followed by a common-source amplifier stage (M_6). The devices M_5 and M_7 form the tail current source for the differential stage and the current source load for the common-source stage. C_c and R_z are the compensation capacitor and the zero-nulling resistor.


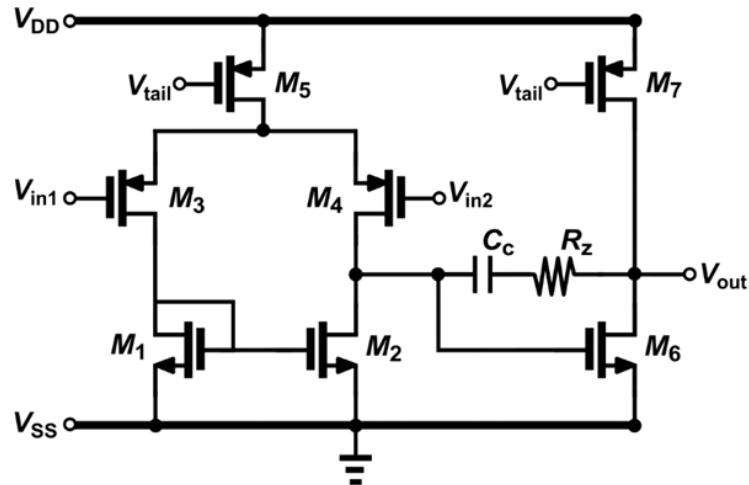


FIGURE 1: A basic two-stage operational amplifier.

TABLE 1: Design specifications @ supply voltage = 1.2V, Load = 100pF, and temperature = 27°C

S.N.	Parameter	Symbol	Value
1.	Open-loop, differential-mode, DC voltage gain	A_0	$\geq 100 \text{ V/V (40 dB)}$
2.	-3dB-Bandwidth	f_{-3dB}	$\geq 5 \text{ MHz}$
3.	Phase margin	PM	$\geq 60^\circ$
4.	Common-mode rejection ratio	$CMRR$	$\geq 30 \text{ dB}$
5.	Power dissipation	P_d	$\leq 800 \mu\text{W}$

Design Steps

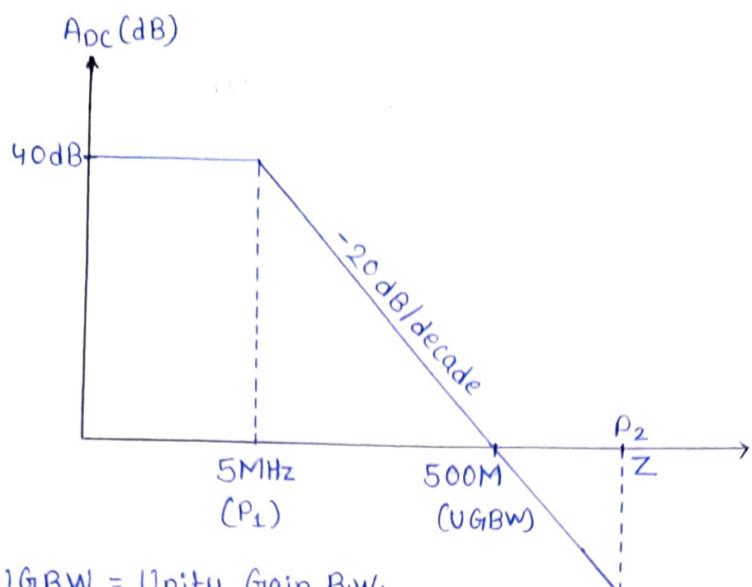

$$\therefore \frac{V_{out}}{V_{in}} = \frac{A_{OC} \left(1 - \frac{s}{Z} \right)}{\left(1 + \frac{s}{P_1} \right) \left(1 + \frac{s}{P_2} \right)}$$

$$\angle \frac{V_{out}}{V_{in}} = -\tan^{-1}\left(\frac{\omega}{Z}\right) - \tan^{-1}\left(\frac{\omega}{P_1}\right) - \tan^{-1}\left(\frac{\omega}{P_2}\right).$$

Take $Z = P_2$

$$\angle \frac{V_{out}}{V_{in}} = -2\tan^{-1}\left(\frac{\omega}{P_2}\right) - \tan^{-1}\left(\frac{\omega}{P_1}\right).$$

$$\angle \frac{V_{out}}{V_{in}} \Big|_{\omega=UGBW} = -2\tan^{-1}\left(\frac{UGBW}{P_2}\right) - \tan^{-1}\left(\frac{UGBW}{P_1}\right)$$

$$UGBW = \frac{g_{m1}}{C_C} = 500 \text{ MHz}$$

$$P_1 \approx \frac{1}{g_{m2} \tau_{02} \tau_{01} C_C}$$

$$P_2 \approx \frac{g_{m2}}{C_L}$$

$$\left. \frac{V_{out}}{V_{in}} \right|_{\omega=GBW} = -2\tan^{-1}\left(\frac{U_{GBW}}{P_2}\right) - \tan^{-1}(g_{m1}g_{m2}\delta_{01}\delta_{02})$$

$$= -2\tan^{-1}\left(\frac{U_{GBW}}{P_2}\right) - \tan^{-1}(A_{DC})$$

$$\therefore -180^\circ + PM = -2\tan^{-1}\left(\frac{U_{GBW}}{P_2}\right) - 90^\circ \quad \because A_{DC} \text{ is very high.}$$

\therefore For $PM = 60^\circ$,

$$\tan^{-1}\left(\frac{U_{GBW}}{P_2}\right) = 15^\circ.$$

$$\therefore \frac{U_{GBW}}{P_2} \approx 0.27$$

$$\therefore P_2 = \frac{500 \text{ MHz}}{0.27} = 1851.85 \text{ MHz.}$$

$$\therefore \frac{g_{m2}}{C_L} = 1851.85 \times 10^6 \times 2\pi$$

Let $C_L = 500 \text{ fF}$ (including parasitics)

$$\therefore g_{m2} \geq 5.85 \text{ mS.}$$

$$U_{GBW} = 500 \text{ MHz}$$

$$\therefore \frac{g_{m1}}{C_L} = 500 \times 10^6 \times 2\pi$$

Let $C_C = 900 \text{ fF}$ (including parasitics).

$$\therefore g_{m1} \geq 2.83 \text{ mS.}$$

$$\therefore R_2 = P_2 \Rightarrow R_2 = \frac{1}{g_{m2}}$$

In our design $g_{m2} = 6.04 \text{ mS}$

$$\therefore R_2 = \frac{1}{6.04 \times 10^{-3}} \approx 165 \Omega.$$

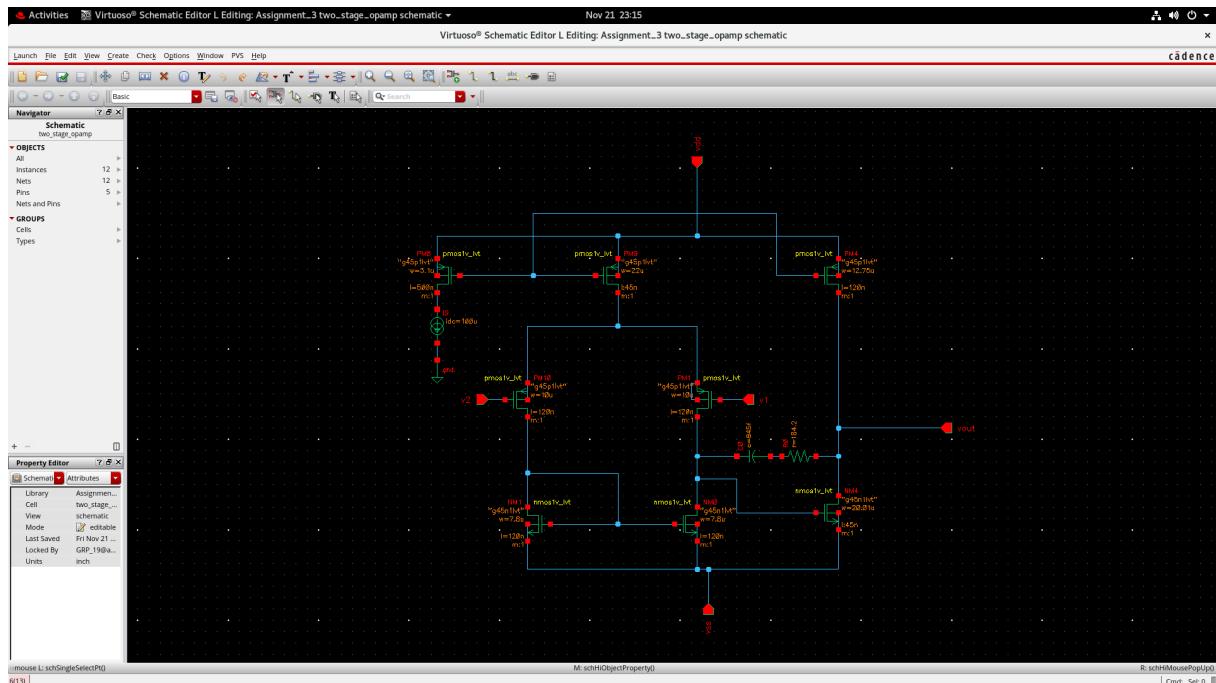


FIGURE 2: Two-stage Opamp

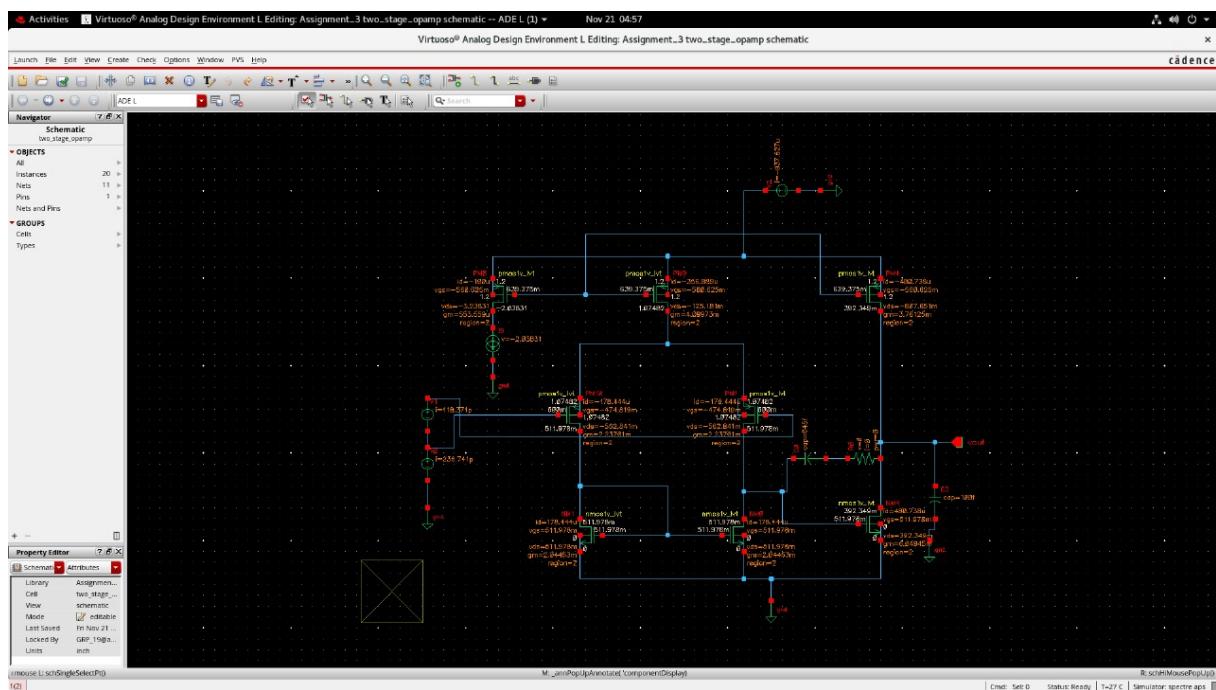
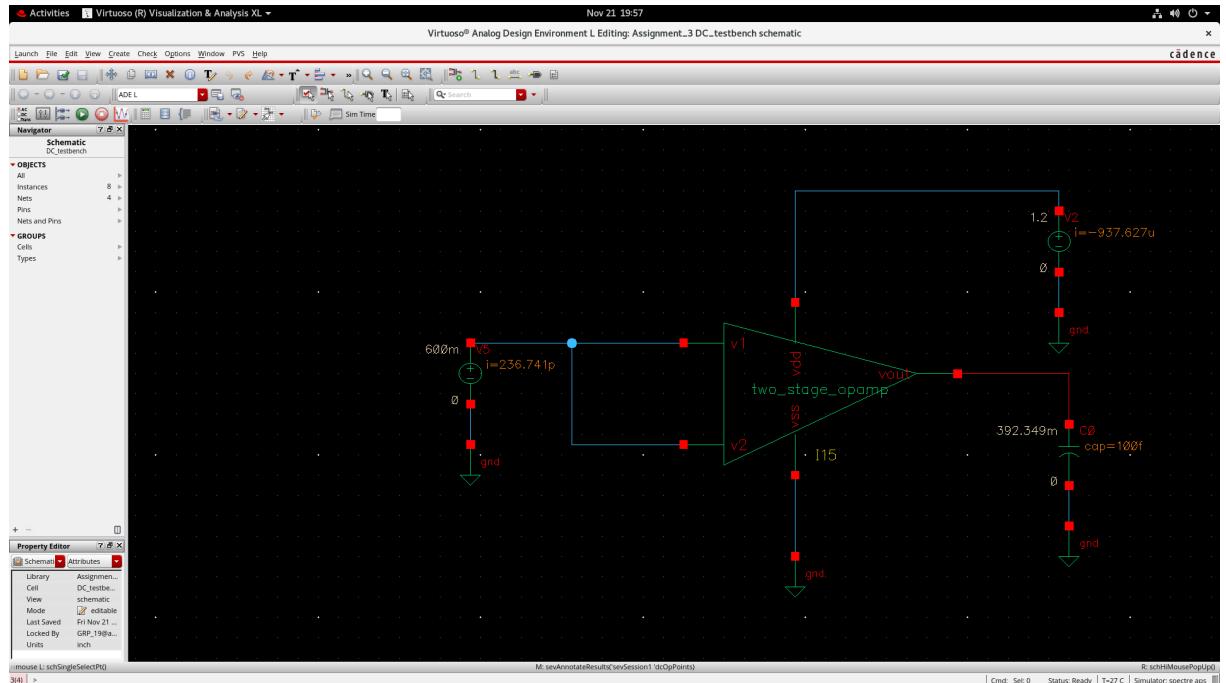
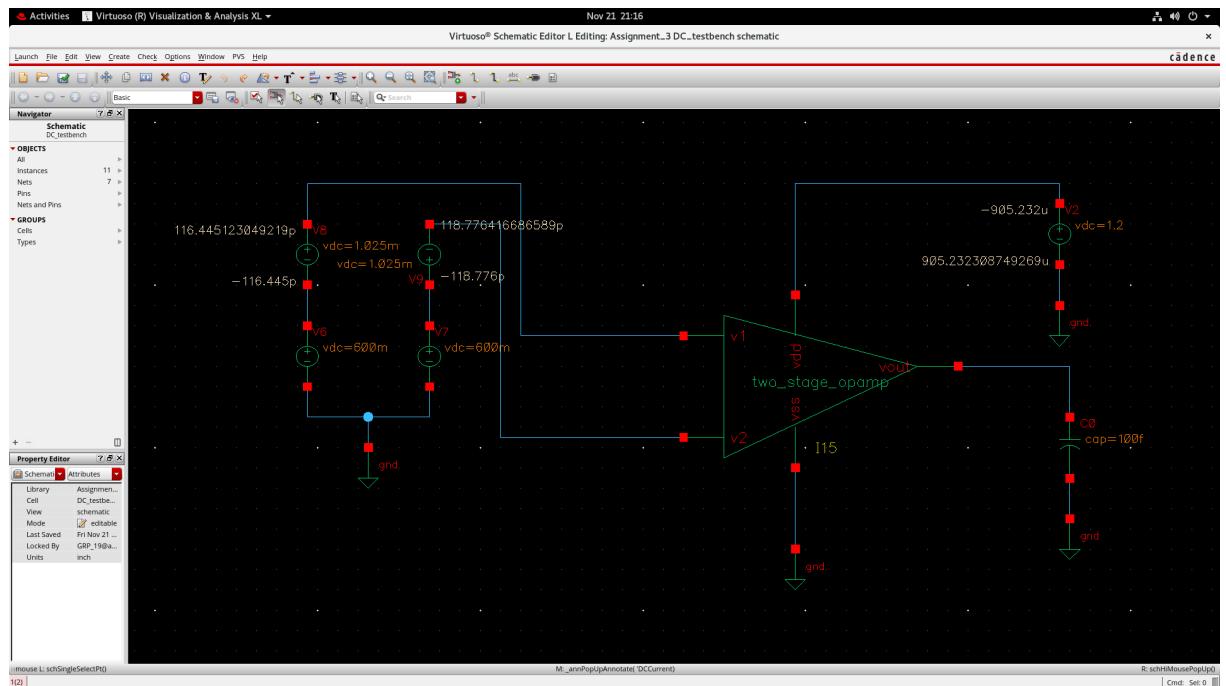


FIGURE 3: DC operating points

0.2 DC Testbench results

FIGURE 4: Opamp with $V_{in} = V_{cm}$ FIGURE 5: Opamp with $V_{in} = V_{id}$

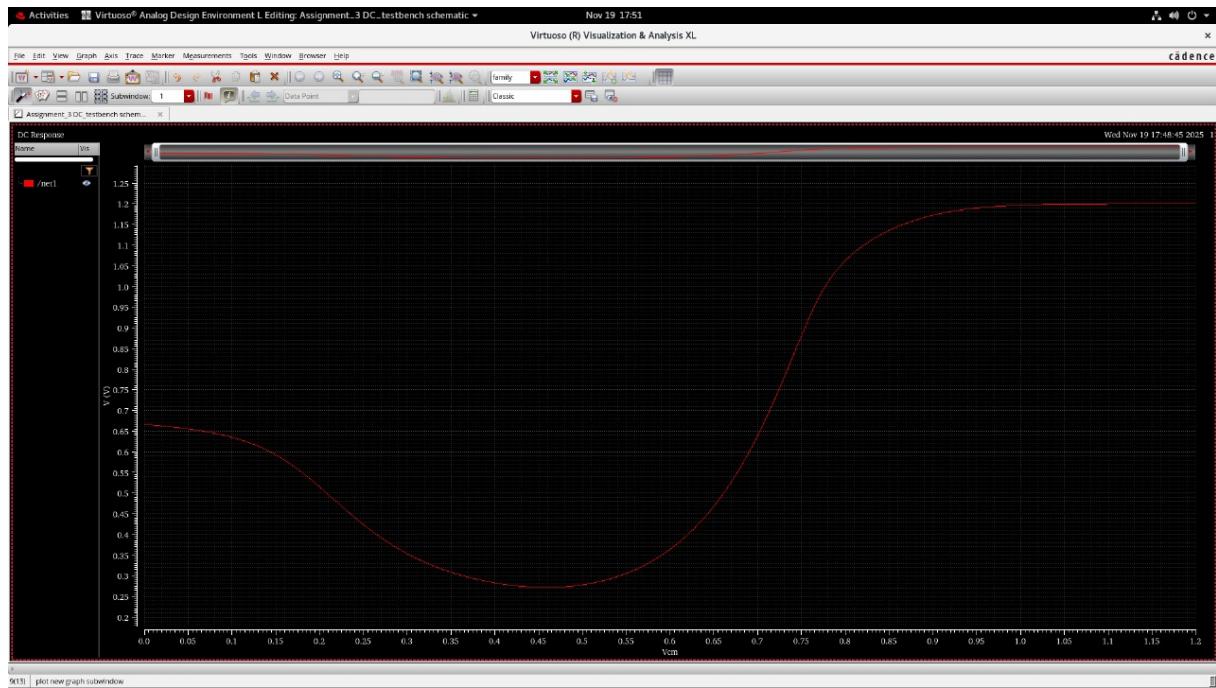


FIGURE 6: CMR Curve

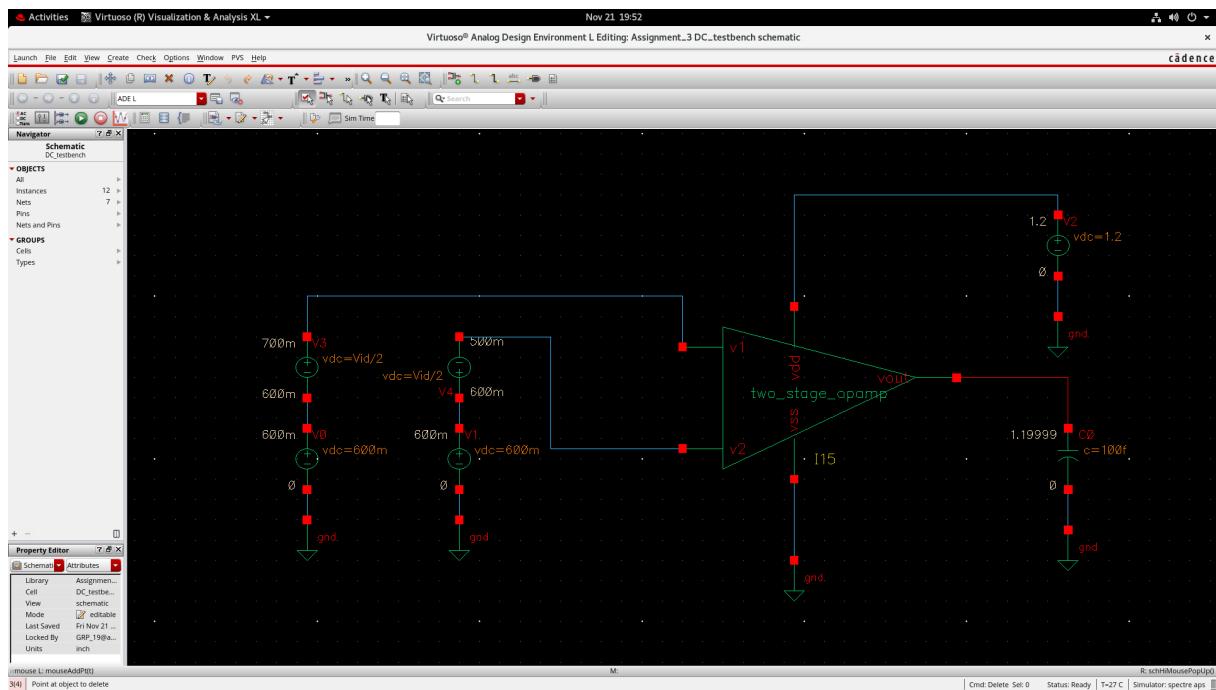




FIGURE 7: VTC Curve with derivative

- $V_{offset} = Vid$ at which $V_{out} = V_{dd}/2 = 600m$
- $V_{offset} = 2.05mV$...from VTC
- $V_1 = V_{cm} + V_{offset}/2$
- $V_1 = V_{cm} - V_{offset}/2$
- DC differential mode voltage gain (A_o) = $600m/2.05m = 292.68$
- DC common mode voltage gain (A_{cmo}) = $392m/600m = 0.653$
- CMRR = $A_o/A_{cmo} = 448.21$ or **53.03 dB**
- $I_{bias,p} = 116.46 \text{ pA}$
- $I_{bias,n} = 118.78 \text{ pA}$
- $I_{bias} = 117.62 \text{ pA}$
- $V_- = 9.22 \text{ mV}$...from VTC
- $V_+ = 1.2 \text{ V}$...from VTC
- Power dissipation = $1.2V \times 937.63\mu\text{A} = 1125.15 \text{ uW}$

0.3 AC Testbench results



FIGURE 8: AC Response for uncompensated opamp


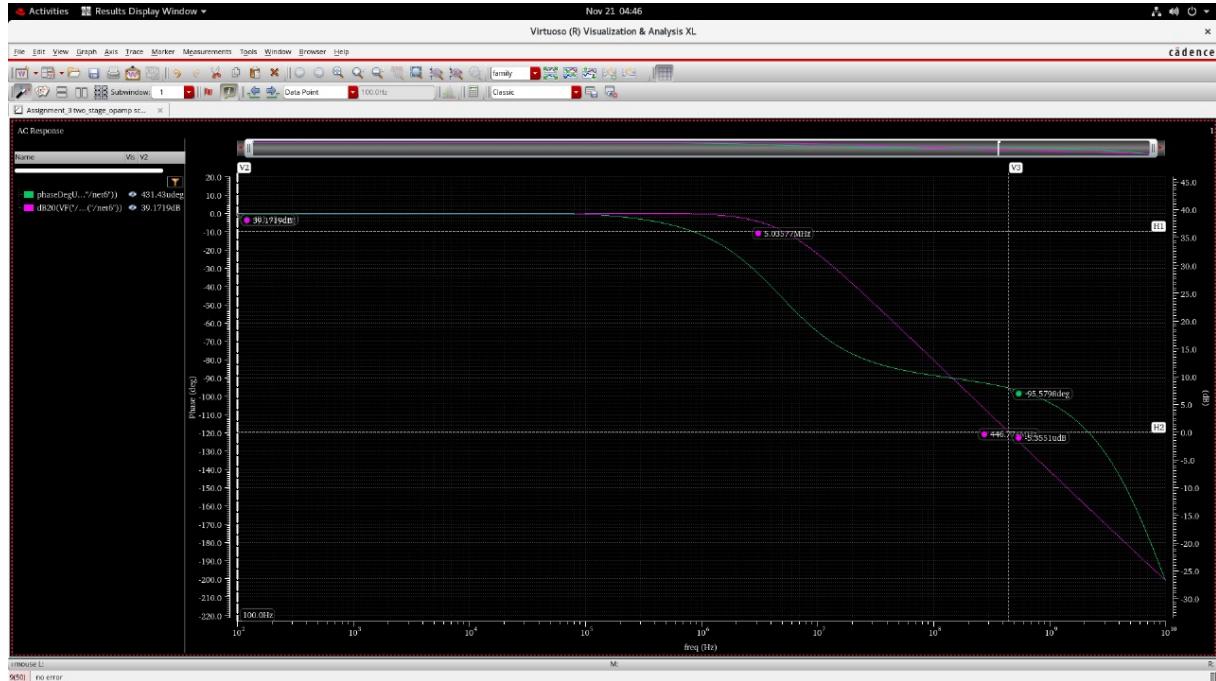


FIGURE 9: AC response of compensated opamp

- DC Voltage gain (A_o) = **39.17dB**
 - -3dB Bandwidth (f_{-3db}) = **5MHz**
 - Gain Bandwidth product (GBW) = **446.77MHz**
 - Phase at 0db = **-95.58 degrees**
 - Phase Margin = $180 - 95.58 = \mathbf{84.42 \text{ degrees}}$

0.4 Transient Testbench analysis

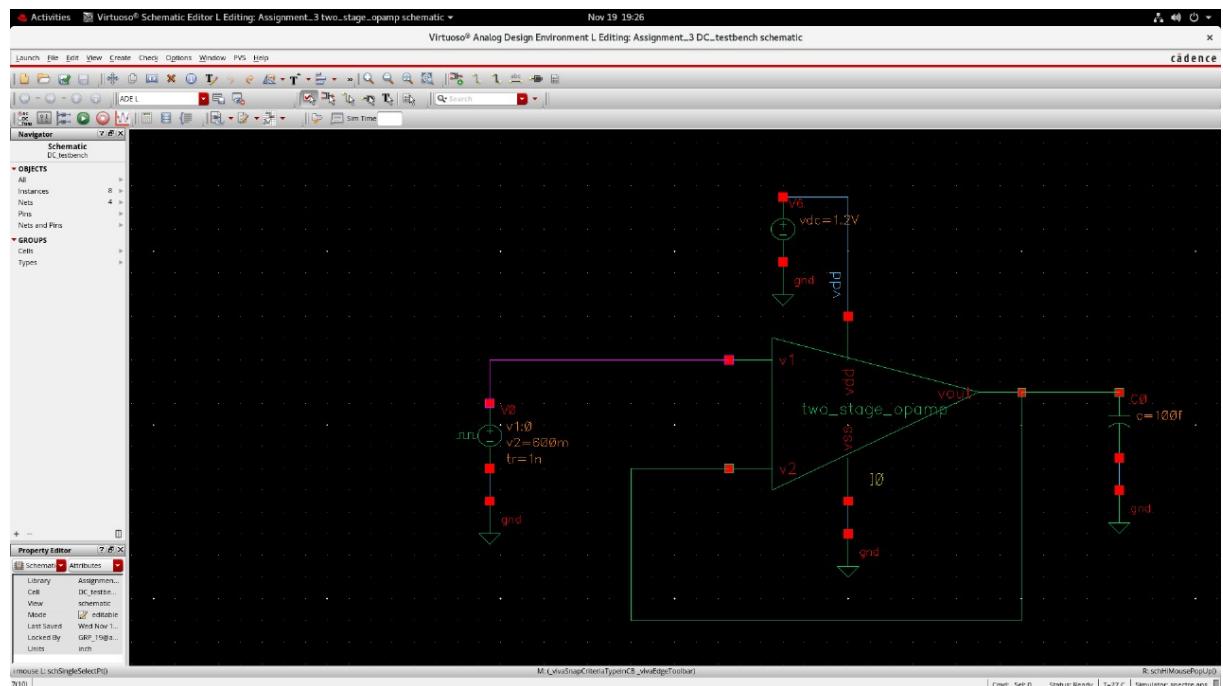

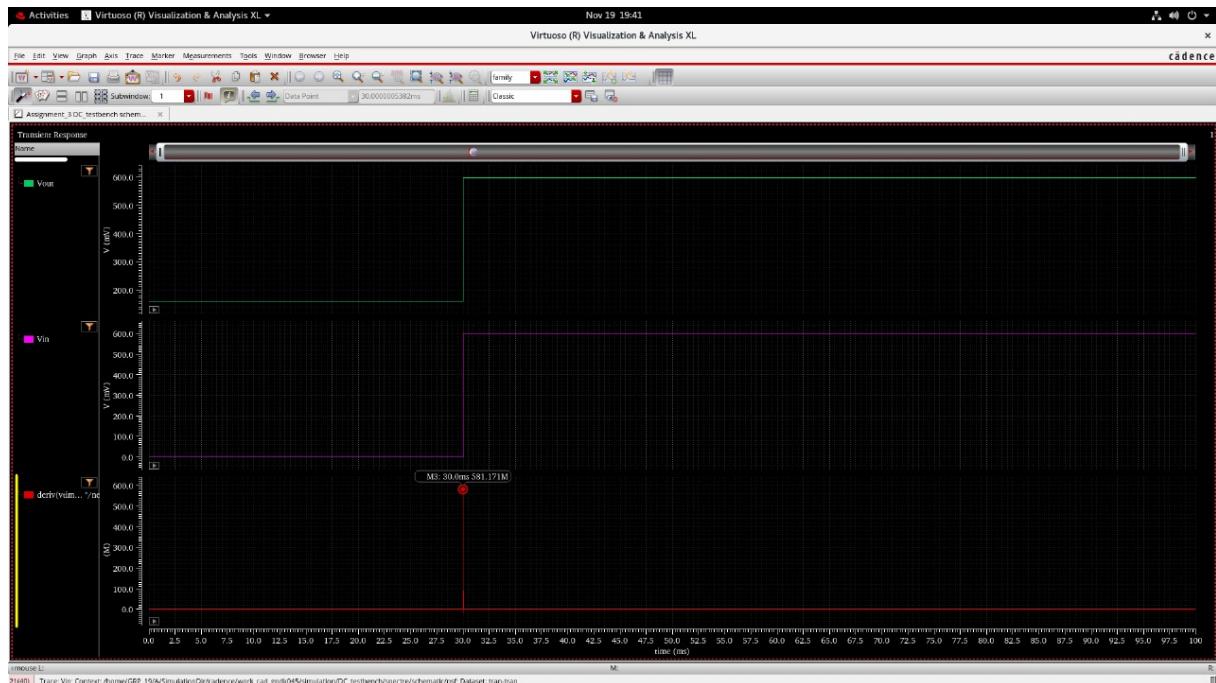


FIGURE 10: Positive step response of compensated opamp

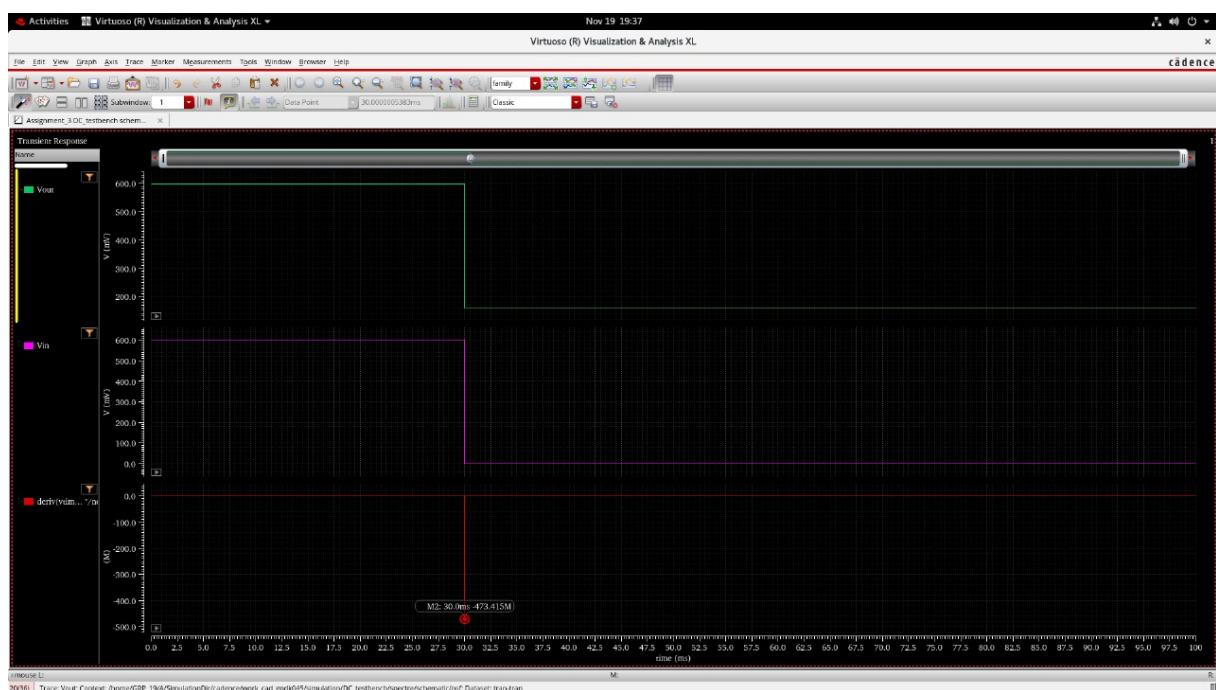


FIGURE 11: Negative step response of compensated opamp

- $SR+ = 581.171 \text{ V/us}$
- $SR- = 473.415 \text{ V/us}$

TABLE 2: Performance parameters of designed two stage op-amp @ [$V_{DD} = 1.2 V$, $C_L = 100 fF$, $T = 27^\circ C$, $V_{ic} = 0.6 V$].

S.N.	Parameter	Symbol	Value
1.	Open-loop, differential-mode, DC voltage gain	A_0	39.17dB
2.	Open-loop, -3 dB bandwidth (with frequency compensation)	f_{-3dB}	5 MHz
3.	Unity-gain frequency or magnitude crossover frequency	f_T or f_{0dB}	446.77 MHz
4.	Phase margin	PM	84.42°
5.	Low-frequency common-mode rejection ratio	$CMRR$	53.03 dB
6.	Power dissipation	P_{diss}	1125.15 μ W
7.	Input-referred offset voltage (systematic)	V_{offset}	2.05 mV
8.	Bias current	I_{bias}	117.62 pA
9.	Slew rate @ 600 mV step	SR^+ SR^-	581.171 V/ μ s 473.415 V/ μ s

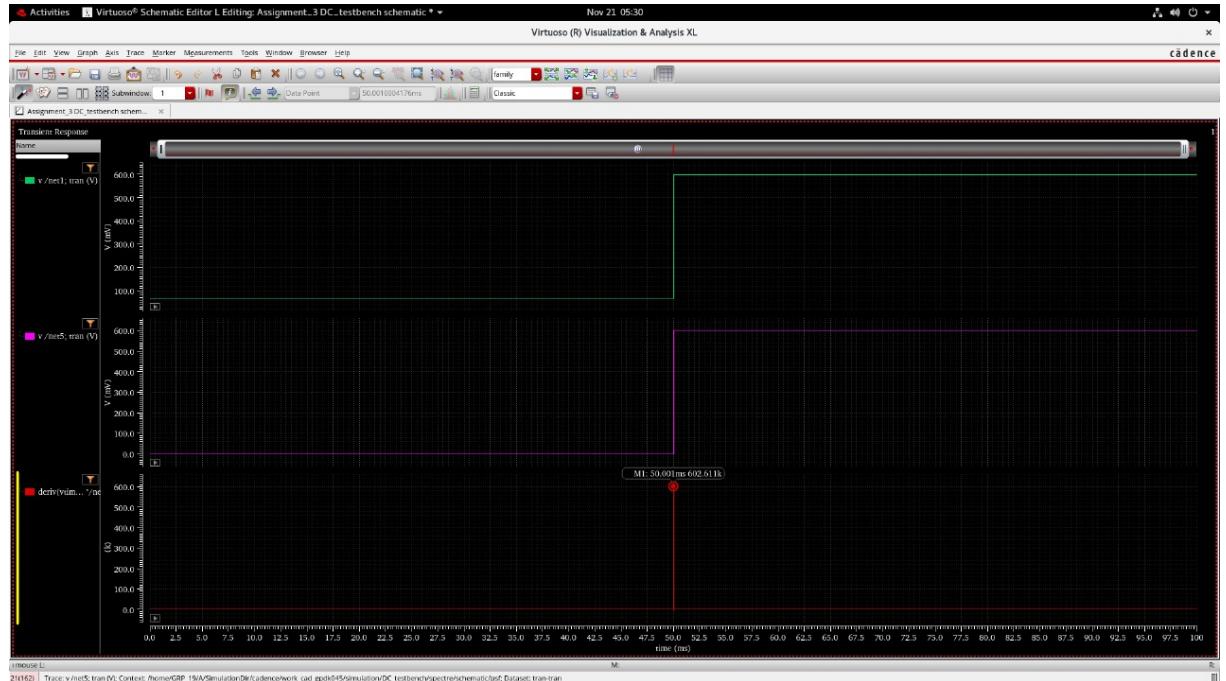


FIGURE 12: Step response of uncompensated opamp

0.5 Include the individual responses in the report to the following:

- Derive the expression for the overall frequency dependent voltage gain from the differential input to the output voltage. Also, write the expression for the gain-bandwidth product

2. The given topology does not include the output stage. Why is it not essential to employ an output buffer in the internal amplifiers?
3. In negative feedback amplifier, explain, in terms of the circuit parameters (not using the feedback theory), the reason for the bandwidth expansion by the factor of one plus loop gain at the expense of the gain reduction by the same factor.