

# E3-277 Introduction to Integrated Circuit Design

## Lab Assignment 3

Submitted

*by*

Group No 19

Dhruv Patel-27096



*under the guidance of*

PROF.GAURAB BANERJEE

DEPARTMENT OF ELECTRICAL COMMUNICATION

ENGINEERING

INDIAN INSTITUTE OF SCIENCE

BENGALURU - 560012

# Contents

<b>Contents</b>	<b>i</b>
<b>List of Figures</b>	<b>iii</b>
0.1 DC Testbench results . . . . .	3
0.2 AC Testbench results . . . . .	4
0.3 Transient Testbench analysis . . . . .	6



# List of Figures

1	A basic two-stage operational amplifier. . . . .	1
2	Two-stage Opamp . . . . .	2
3	DC operating points . . . . .	2
4	DC Transfer curve . . . . .	3
5	Voltage Transfer Characteristic . . . . .	3
6	AC response of compensated opamp . . . . .	4
7	Common mode gain . . . . .	5
8	Positive step response of compensated opamp . . . . .	6
9	Negative step response of compensated opamp . . . . .	7



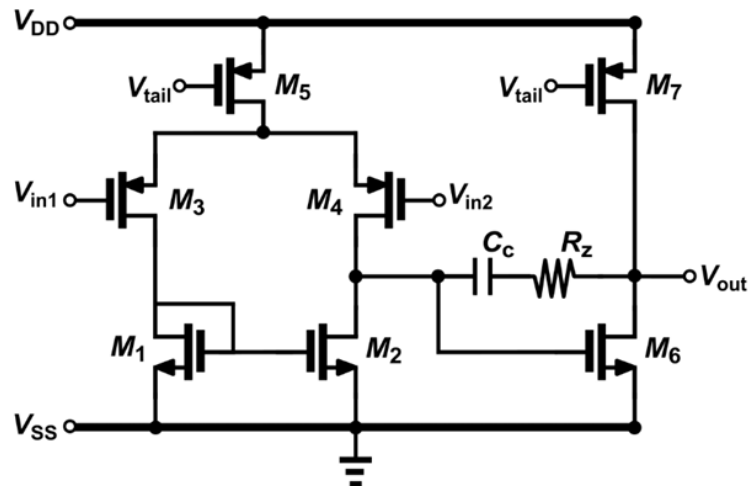


FIGURE 1: A basic two-stage operational amplifier.

TABLE 1: Design specifications @ supply voltage = 1.2V, Load = 100pF, and temperature = 27°C

S.N.	Parameter	Symbol	Value
1.	Open-loop, differential-mode, DC voltage gain	$A_0$	$\geq 100 \text{ V/V (40 dB)}$
2.	-3dB-Bandwidth	$f_{-3dB}$	$\geq 5 \text{ MHz}$
3.	Phase margin	$PM$	$\geq 60^\circ$
4.	Common-mode rejection ratio	$CMRR$	$\geq 30 \text{ dB}$
5.	Power dissipation	$P_d$	$\leq 800 \mu W$

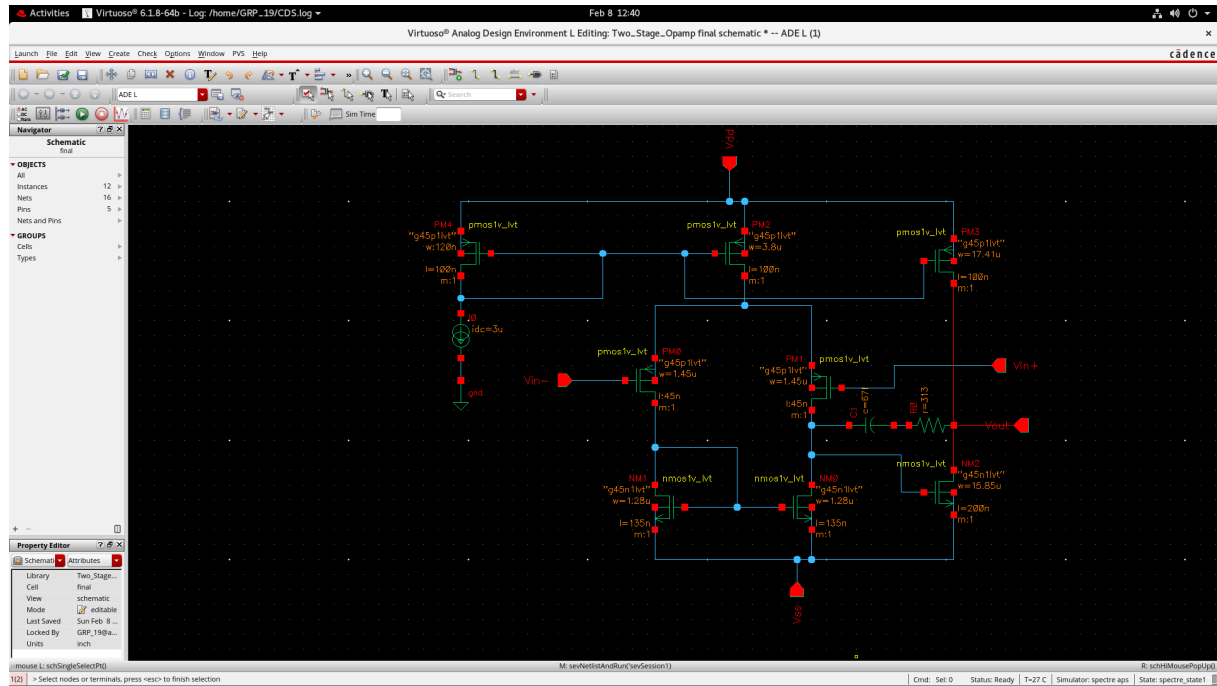


FIGURE 2: Two-stage Opamp

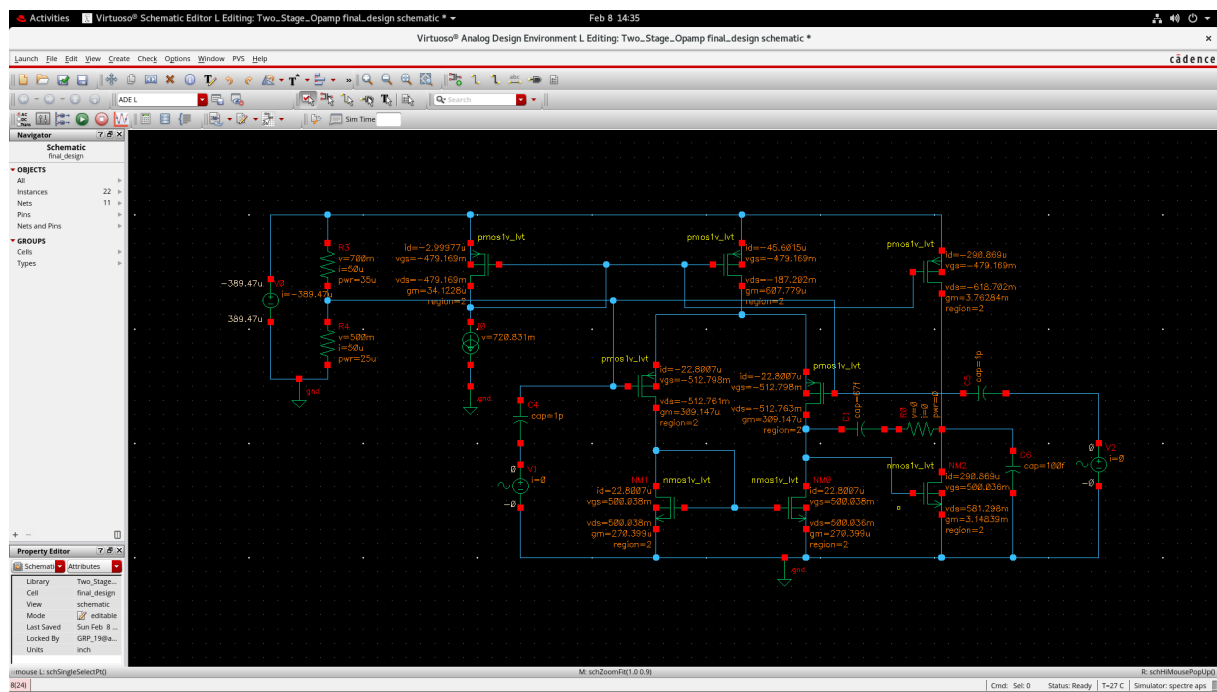


FIGURE 3: DC operating points

## 0.1 DC Testbench results

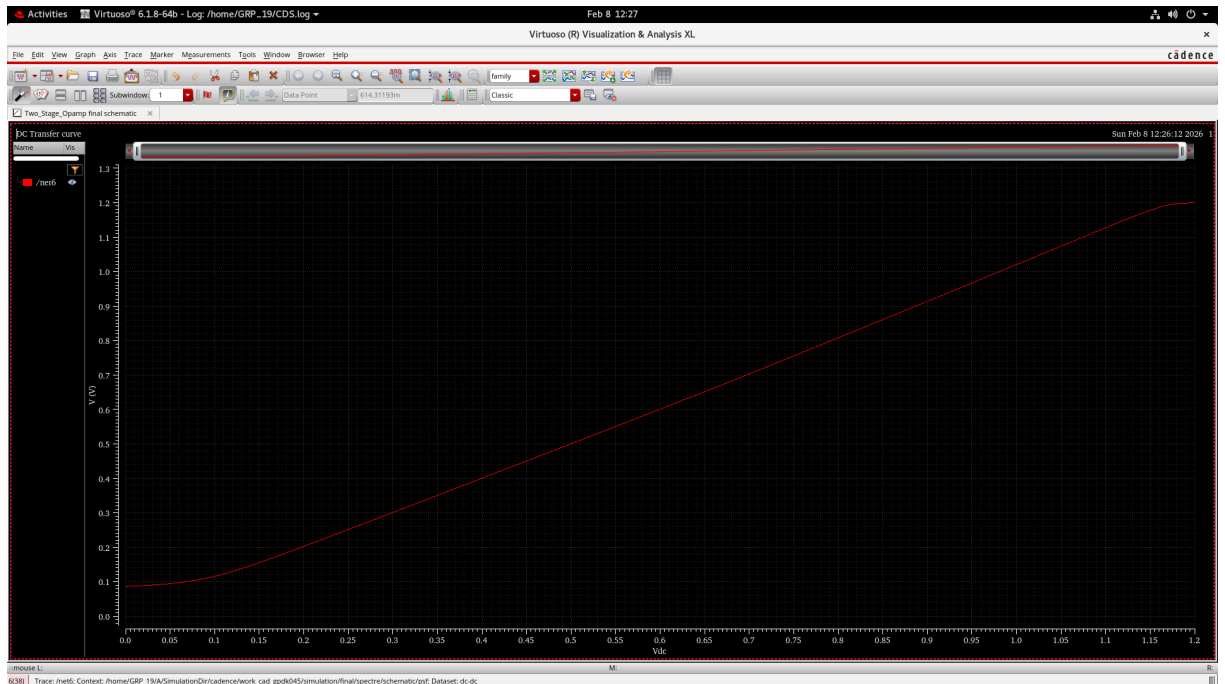


FIGURE 4: DC Transfer curve

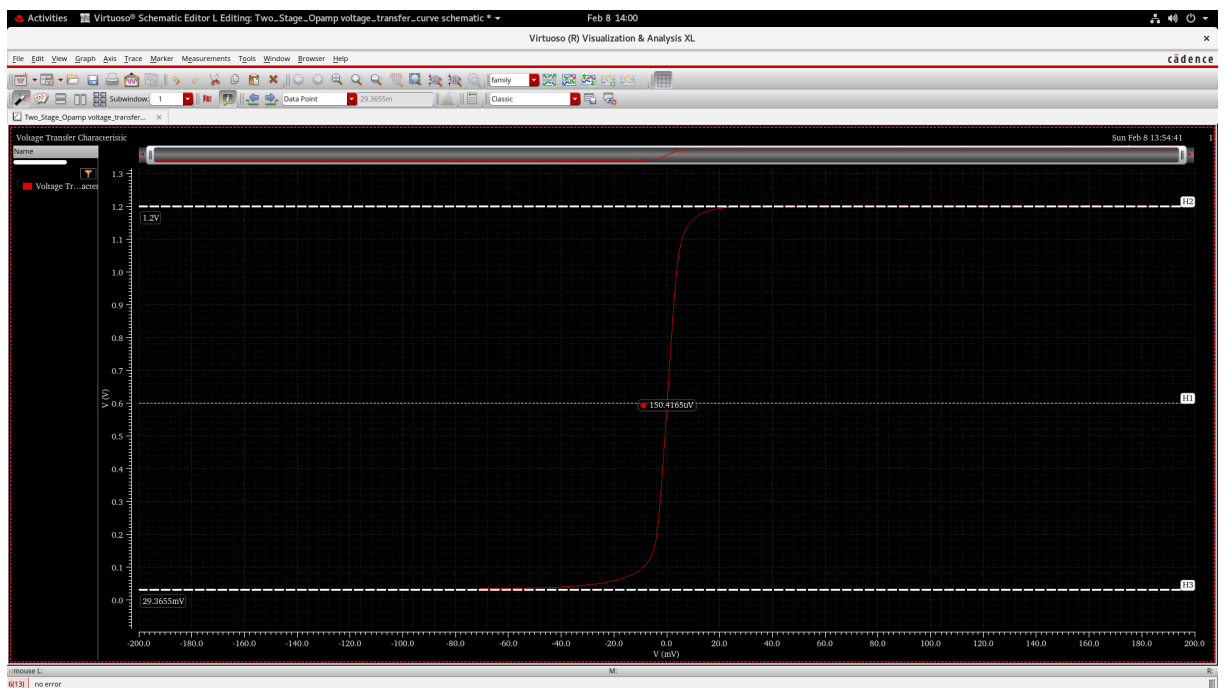


FIGURE 5: Voltage Transfer Characteristic



- $V_{\text{offset}} = V_{\text{id}}$  at which  $V_{\text{out}} = V_{\text{dd}}/2 = 600\text{m}$
- $V_{\text{offset}} = \mathbf{150.4165\mu V}$  ...from VTC
- Power dissipation =  $1.2\text{V} \times 389\mu\text{A} = \mathbf{467.364\text{ uW}}$

## 0.2 AC Testbench results

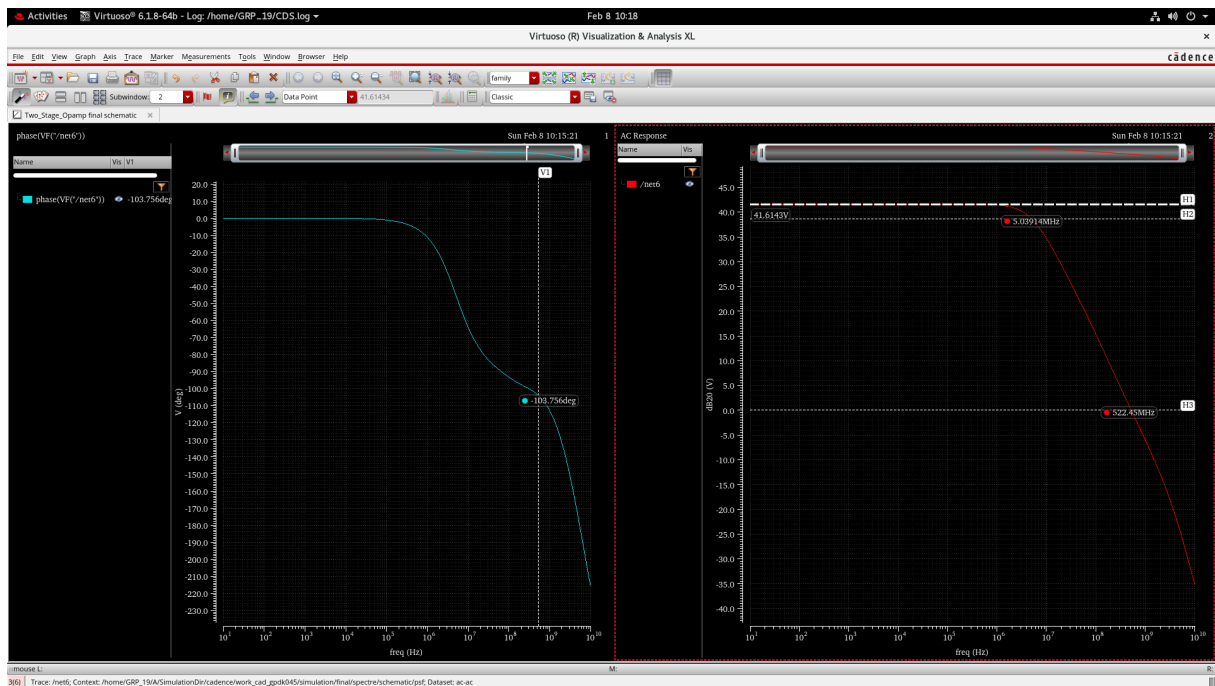


FIGURE 6: AC response of compensated opamp

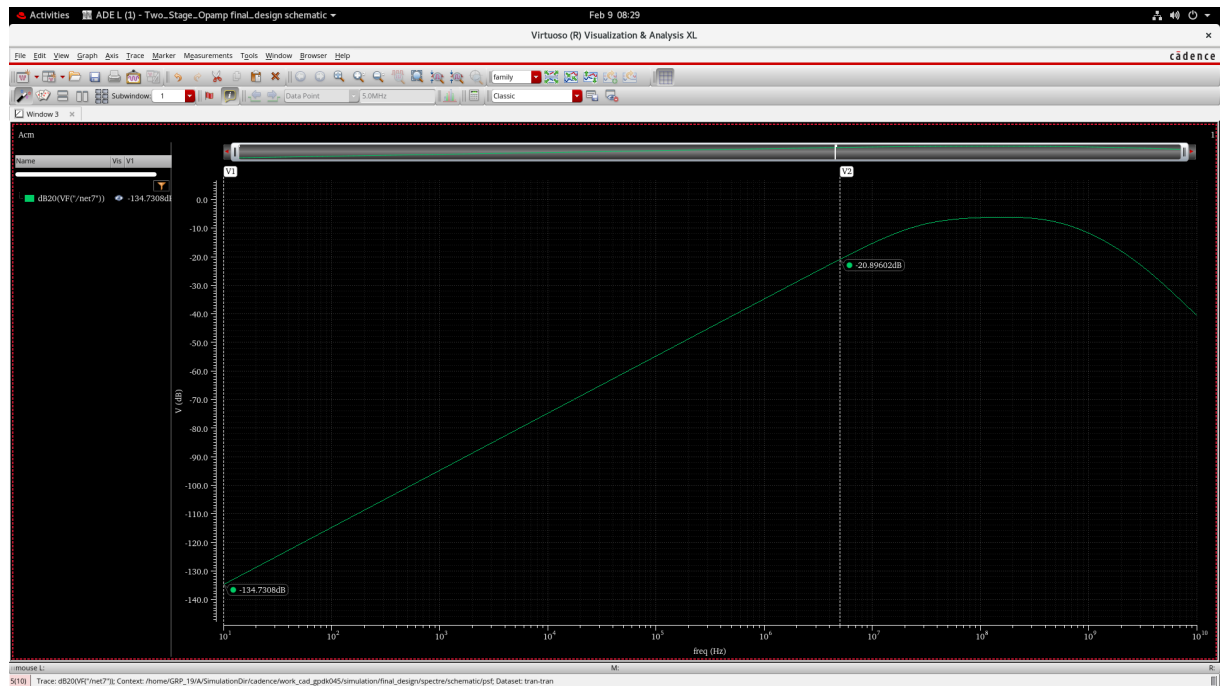


FIGURE 7: Common mode gain

- DC Voltage gain ( $A_o$ ) = **41.6143dB**
- -3dB Bandwidth ( $f_{-3db}$ ) = **5.039MHz**
- $A_{cm}$  at 5MHz = -20.89602dB
- CMRR at 5MHz =  $A_d - A_{cm} = 41.6143 - (-20.8960) =$  **62.5103 dB**
- Gain Bandwidth product (GBW) = **522.45MHz**
- $\text{Phase}_{0db} = -103.765^\circ$
- Phase Margin =  $180 - 95.58 = 76.235^\circ$

## 0.3 Transient Testbench analysis


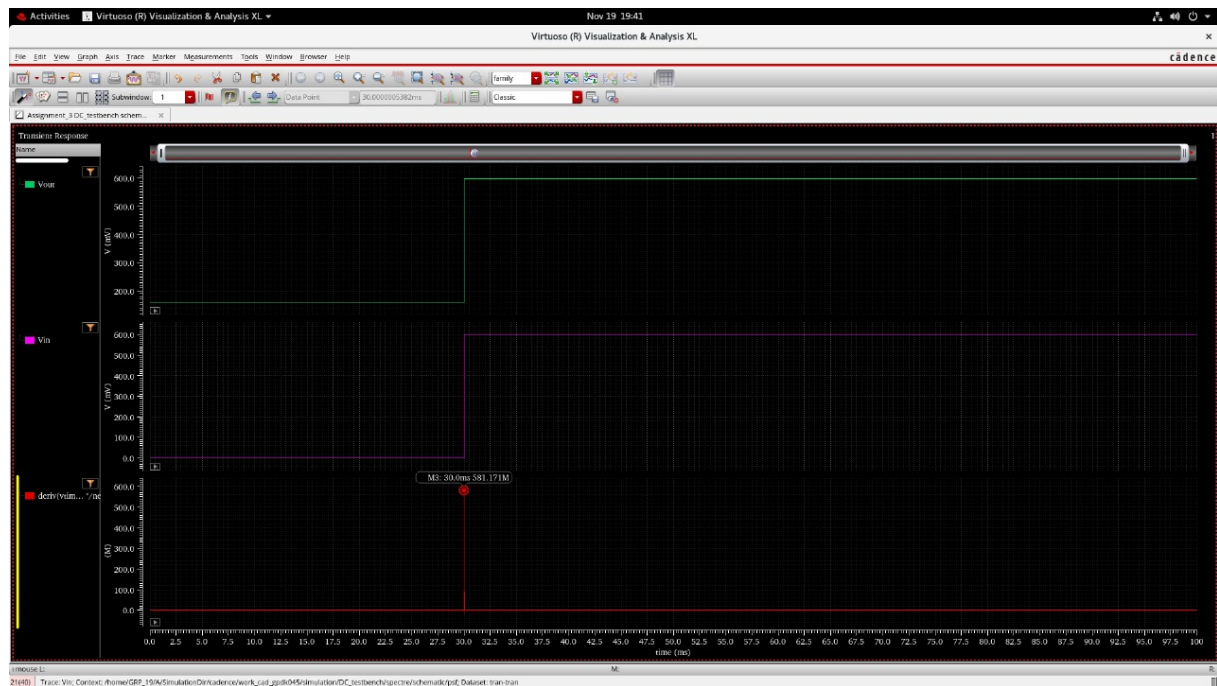


FIGURE 8: Positive step response of compensated opamp

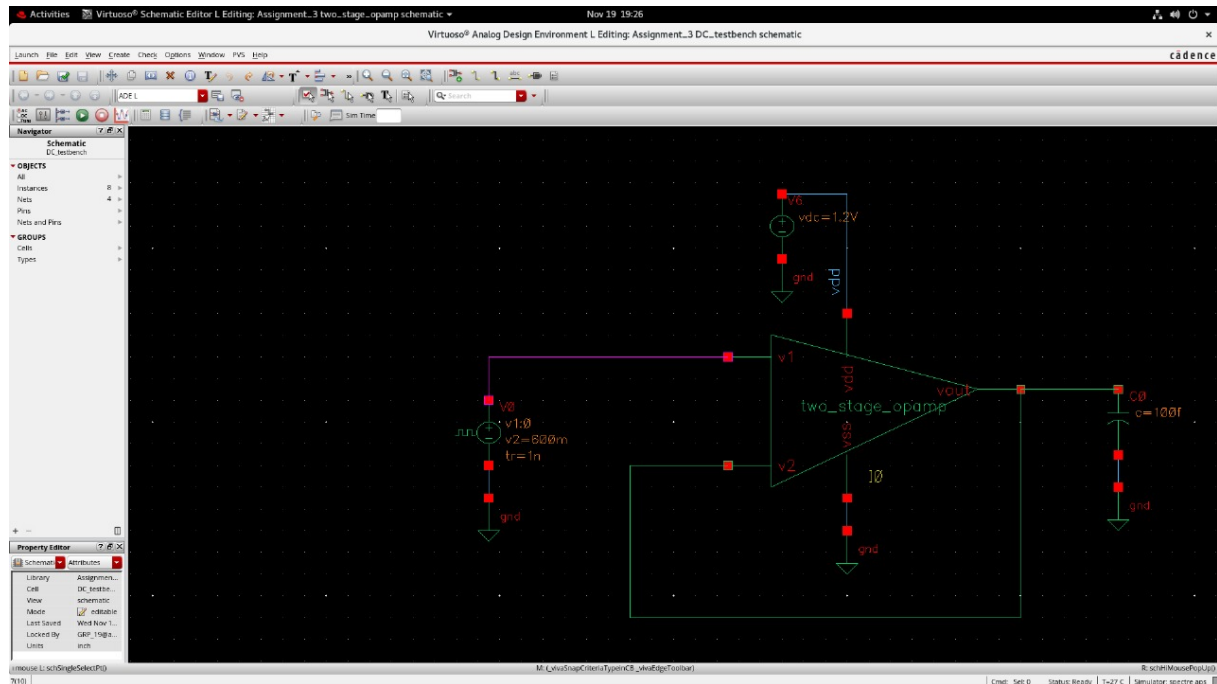

FIGURE 9: Negative step response of compensated opamp

- $SR^+ = 581.171 \text{ V}/\mu\text{s}$
- $SR^- = 473.415 \text{ V}/\mu\text{s}$

TABLE 2: Performance parameters of designed two stage op-amp @  $[V_{DD} = 1.2 \text{ V}, C_L = 100 \text{ fF}, T = 27^\circ\text{C}, V_{ic} = 0.6 \text{ V}]$ .

S.N.	Parameter	Symbol	Value
1.	Open-loop, differential-mode, DC voltage gain	$A_0$	41.6143d
2.	Open-loop, -3 dB bandwidth (with frequency compensation)	$f_{-3dB}$	5.039 MHz
3.	Unity-gain frequency or magnitude crossover frequency	$f_T$ or $f_{0dB}$	522.45 MHz
4.	Phase margin	$PM$	76.235°
5.	Low-frequency common-mode rejection ratio (10Hz to 5MHz)	$CMRR$	> 61.51 dB
6.	Power dissipation	$P_{diss}$	467.364 $\mu\text{W}$
7.	Input-referred offset voltage (systematic)	$V_{offset}$	150.4165 $\mu\text{V}$
9.	Slew rate @ 600 mV step	$SR^+$ $SR^-$	581.171 V/ $\mu\text{s}$ 473.415 V/ $\mu\text{s}$